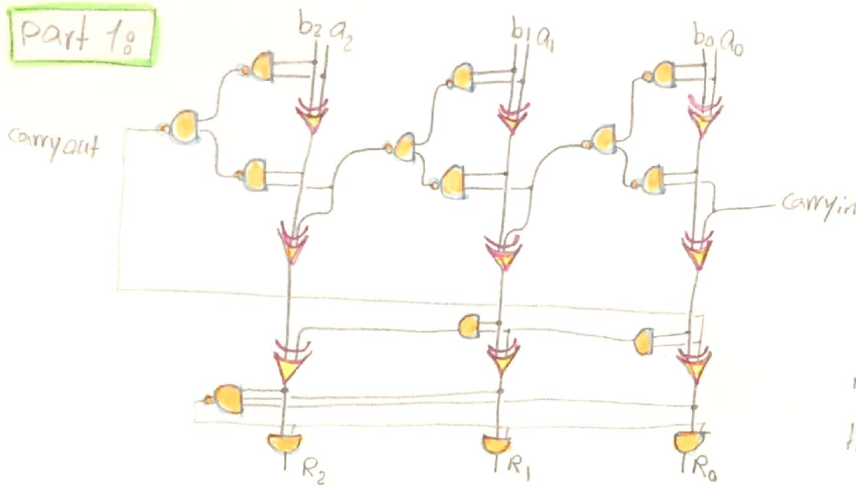


Part 1:




XOR #18ns NOT #6ns
 NAND(3) #12ns NAND(2) #8ns
 worst case Delay # $18 + 16 + 16 + 16 + 14 + 14 + 18 + 12 + 14 = 38ns$

inputs → 3-bit a - 3-bit b carryin


outputs → 3-bit R

in this part we have a residue-7 to show us the result of operation

Part 2:

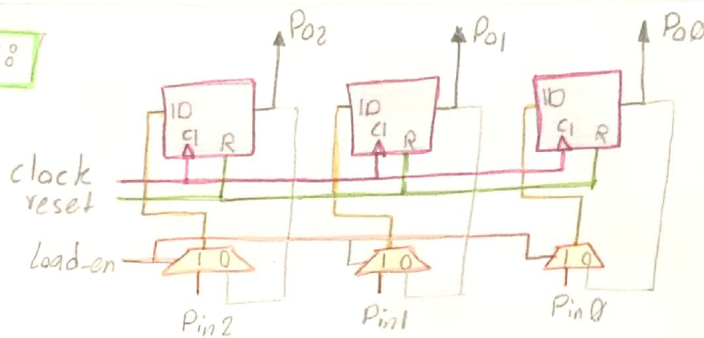


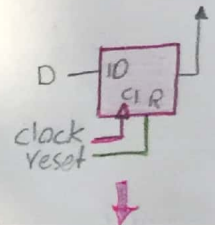
delay flip flop #
 $12 + 12 + 12 + 8 = 44ns$



worst case delay = worst case delay mux
 + worst case delay flip flop = $22 + 44 = 66ns$

in this part we designed a circuit with (inputs → reset - clock - load-en - 3-bit Pin) (outputs → 3-bit Pout). This circuit can save our data that we gave.

Part 3:

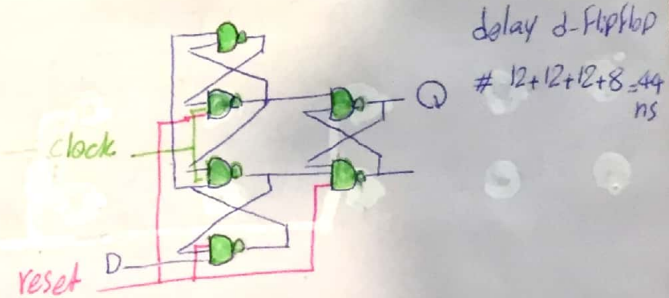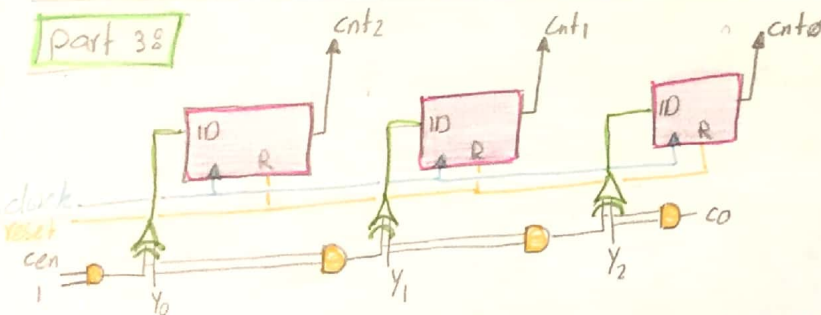


worst case Delay of a flip flop # from last Part = 44ns (co delay # $14 + 14 + 14 + 14 = 56ns$)

worst case Delay of this circuit (3-bit up counter) → delay count = $14 + 14 + 14 + 18 + 4 + 4 = 104ns$

In this part we made a 3-bit up counter that can count from 000 to 111 (0 to 7) modulo-8 binary up-counter with (input → count enable - rising edge clock - an asynchronous reset = cin and output → carry out) total delay = delay flip flop + delay xor gate + and

Part 4:

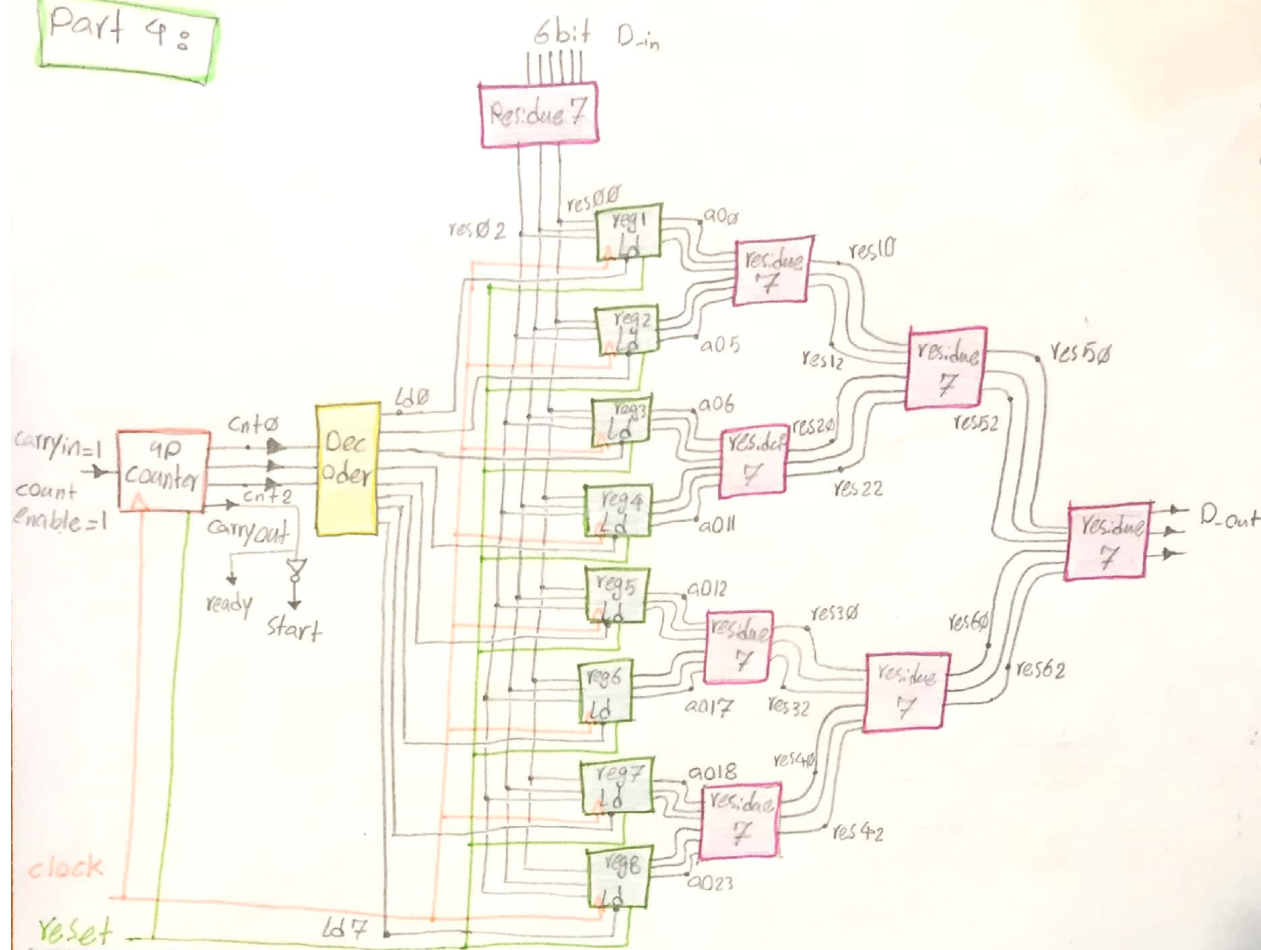

in this part we designed a 48-bit residue 7 circuit. the 48-bits of data for this circuit come in 6-bit chunks.

inputs: } reset
clock
6-bit D-in

outputs: } 3-bit D-out
start

Part 5:

in this part we passed all of 48-bit to the residues with suitable we set each inputs to drive residue. in this case we also set the reset on one cycle. in order to make a unexpensive circuit, we only used a Residue-7 & give our inputs to the residue step by step so we have a residue & 8 register which is controlled by a upcounter & a decoder instead of 8 residues. in this part we need to give the 6-inputs of 48-inputs before press the clock as we need the ~~add~~ for the initial value in our circuit so we press the reset to become 1 & D-out becomes 3-bit 0. then we give the inputs, for example first 6-bits = 58 and second 6-bits = 8 & = 63, 10, 12, 2, 50. & 9 in decimal numbers. so they are our first residue inputs & output of every 6-bit inputs is 3 bit that named res0. every 3-bits of our out put is given to a single register for storing our result that we need to give to other residues. in this example our final result is 2 = 010 (in binary num.). the start signal is 1 when our circuit is ready to show us the final result & it's become 0 when the output shows us the final result.