

part 1)

output m3 is $w_m = (a \& b) \& c$

in this structure we use 14 transistor.

in a CMOS structure that called MA3

we use six wires for simulate

The Design and a,b,c main input

and 1 output called w_m .


pullup And pulldown design correctly

As you see.

but in code \Rightarrow All of details of design transfer into code

in switch level for example

 $\Rightarrow \begin{cases} \text{nmos} \#(3,4,5) \text{ T1 (drain, source, control)} \\ \text{pmos} \#(5,6,7) \text{ T2 (drain, source, control)} \end{cases}$




\Rightarrow After simulate the design I have a test bench that gets three inputs and 1 output the delay Assign arbitrary and in last step we will see the wave form and analyze the wave.

part 2-1

2-input NAND

in this part we have a CMOS 2-nand structure

 $\begin{cases} \text{input} \Rightarrow a, b \\ \text{wire} \Rightarrow \text{wire 1} \\ \text{output} \Rightarrow w \end{cases}$



I design that in a NAND module. AND with 4 Transistor


2nmos and 2pmos with given delay I complete the circuit. After That we assign values to every input and output in TB and in last part we analyze the wave.

calculate delay for 2-input NAND \Rightarrow

$\begin{cases} \text{nmos} \#(3,4,5) \\ \text{pmos} \#(5,6,7) \end{cases} \Rightarrow \text{delay} \begin{cases} \text{To } 0 \Rightarrow * 8\text{ns} \\ \text{To } 1 \Rightarrow * 10\text{ns} \end{cases}$

3-input NAND

(part 2-2)

 



in this part we have a CMOS 3-input structure $\begin{cases} \text{input} \Rightarrow a, b, c \\ \text{wire} \Rightarrow \text{wire 1, wire 2} \\ \text{output} \Rightarrow \text{output} \end{cases}$

in this part I repeat all of work which done in previous section.

calculate delay for 3-input NAND \Rightarrow

$\begin{cases} \text{nmos} \#(3,4,5) \\ \text{pmos} \#(5,6,7) \end{cases} \Rightarrow \begin{cases} \text{To } 0 \Rightarrow * 12\text{ns} \\ \text{To } 1 \Rightarrow * 15\text{ns} \end{cases}$

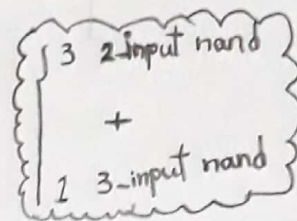 part 3) After make a oros gate we have a circuit with only NAND gates.



in this part we replace AND with a NAND+NOT it concluded a circuit like Figure above.

modulesim has NAND primitives with below syntax.

NAND #(To1,To0) name(out1,in1,in2,...). in last step I use the value delay for nand obtained in part 2 as you see in my code. After that the action of assign value in testbench will done and the analyze wave is the last step for us :)

part 4) we have a testbench that contain both MAJ(1 & 3) with same inputs. After simulate Andran

we have 2 wave-form. difference of two waves are related to delay and accuracy

The time between to 1 in both waves is Almost 10ns.

and the accuracy of MAJ2(switch level) is better than MAJ3 (gate level)

part 5) in this part we learn how to use Assign to make a optimum output of MAJ (MAJ5)

in this part we extract the delay from wave of MAJ1 [switch level] then use these delay in place of

two delay value of assign structure.

these delay $\Rightarrow \begin{cases} T_{01} = 26\text{ns} \\ T_{10} = 22\text{ns} \end{cases} \Rightarrow \underline{\text{extract from wave}}$



but in code \Rightarrow After use Assign to make structure MAJ we have problem with testbench.

intestbench we declare MAJ1(part I) and MAJ5 and the last step is assign value for inputs and output

with Analyze the wave MAJ1 we extract the delay and use them as parameters of assign

part 6)

XOR 3input

  

in this part we should calculate the delay for above circuit called XOR 3-input

delay not gate $\begin{cases} \text{To 0} & 7\text{ns} \\ \text{To 1} & 5\text{ns} \end{cases}$

the worst case delay $\begin{cases} \text{To 1} \Rightarrow \text{worst path} \Rightarrow 3*5 + \text{worst not}(7\text{ns}) = 22\text{ns} \\ \text{To 0} \Rightarrow \text{worst path} \Rightarrow 3*7 + \text{worst not}(5\text{ns}) = 26\text{ns} \end{cases}$

in my code \Rightarrow like part 5, I use assign to make ODD structure with delay value which calculate above and after that we have a module ODD-TB that used to assign value to inputs and output just like always we analyze the wave. and

part 7) in this part I use a test bench and declare both MAJ and ODD structure with same input a, b, c and output r for MAJ & output s for ODD and analyze both wave form in simulation of modulesim.

The results shows that MAJ and ODD are complementary this mean when output of MAJ is zero the output of ODD is one. (Except in 000 & 111)

this result shown in figures.

a	b	c	MAJ(r)	ODD(s)
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	0	1
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	0